

# Chapter 2: Direct Current Meters

**Dr. Muna HajjYahya**  
**Dr. Maen Ishtaiwi**

Physics Department  
An-Najah National University  
**Electrical Instrumentation**



February 1, 2019


# Contents

- 1 D'Arsonval Meter Movement
- 2 D'Arsonval Meter as DC Ammeter
- 3 Multi-range Ammeter (The Ayrton Shunt)
- 4 Ammeter Insertion Effect
- 5 D'Arsonval Meter as DC Voltmeter
- 6 Multi-Range DC Voltmeter
- 7 Voltmeter Loading Effects
- 8 The Ohmmeter

# 1. D'Arsonval Meter Movement


- Also called Permanent-Magnet Moving Coil (PMMC).
- Based on the moving-coil galvanometer constructed by d'Arsonval in 1881.
- Can be used to indicate the value of DC and AC quantity.
- Basic construction of modern PMMC can be seen in the Figure (see next slide).

# D'Arsonval Meter Movement

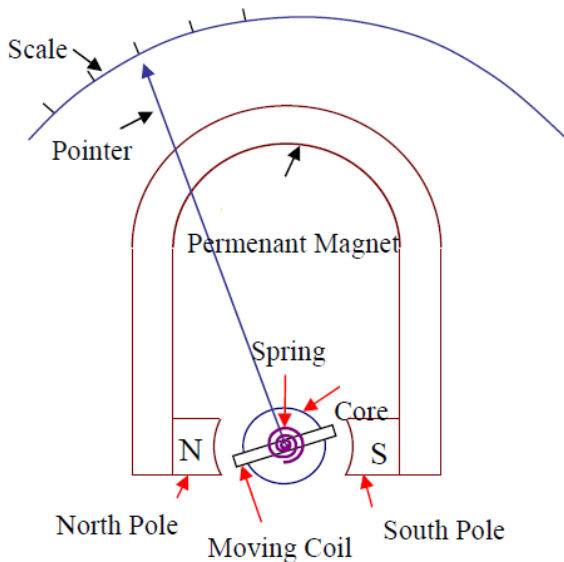

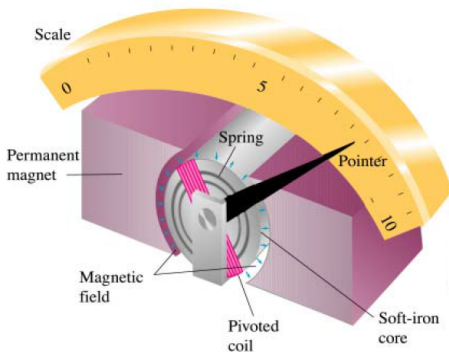
# Operation D'Arsonval Meter

- When current flows through the coil, the core will rotate.
- Amount of rotation is proportional to the amount of current flows through the coil.
- The meter requires low current ( $50\mu\text{A}$ ) for a full scale deflection.
- Its accuracy is about 2% - 5% of full scale deflection.



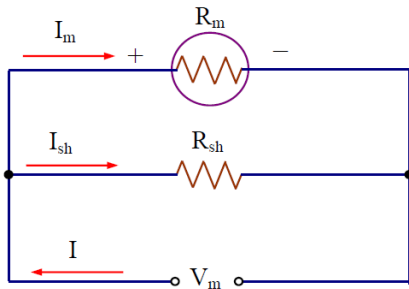
## 2. D'Arsonval as DC Ammeter

- The PMMC galvanometer constitutes the basic movement of a DC ammeter.
- The coil winding of a basic movement is small and light, so it can carry only very small currents.
- A low value resistor (shunt resistor) is used in DC ammeter to measure large current.
- Basic DC ammeter:


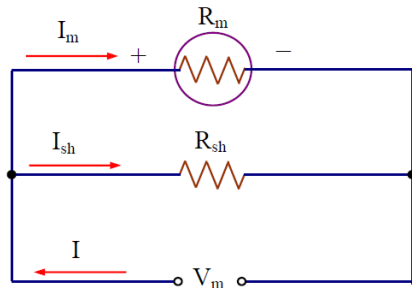
# D'Arsonval as DC Ammeter

- $R_{sh}$ : resistance of the shunt.
- $R_m$ : internal resistance of the meter movement (resistance of the moving coil).
- $I_{sh}$ : current through the shunt.
- $I_m$ : full scale deflection current of the meter movement.
- $I$ : full scale current of the ammeter + shunt (i.e. total current).



## Example 1

Calculate the value of the shunt resistance required to convert a 1 mA meter movement, with a  $100\ \Omega$  internal resistance, into 0 to 10 mA ammeter.




## Example 2

A  $100\ \mu\text{A}$  meter movement with an internal resistance of  $800\ \Omega$  is used in a 0 to 100 mA ammeter. Find the value of the required shunt resistance?

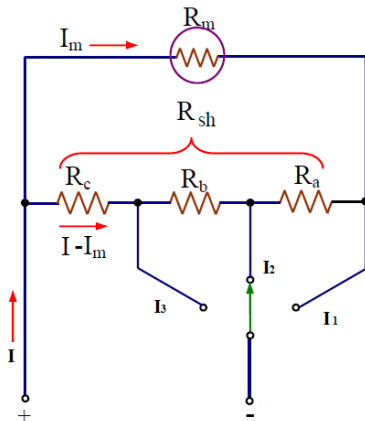
### 3. Multi-range Ammeter (The Ayrton Shunt)

- The shunt resistance works well enough on a single-range ammeter.
- On a multiple-range ammeter, the **Ayrton shunt** is frequently a more suitable design.
- The **Ayrton shunt** circuit is shown in the figure


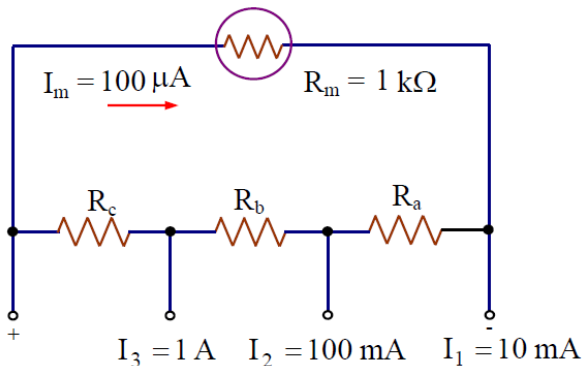
## Example 3

Compute the value of the shunt resistors for the circuit shown in the Figure.




## 4. Ammeter Insertion Effect

- Inserting Ammeter in a circuit always increases the resistance of the circuit and, thus always reduces the current in the circuit. The expected current:

$$I_e = \frac{E}{R_1} \quad (1)$$

where;

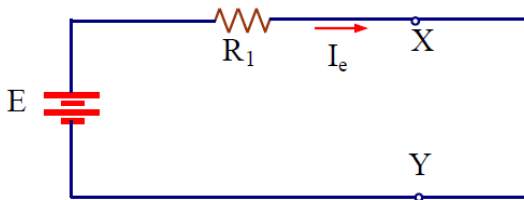$I_e$ : the expected current, is the current **without** the ammeter in the circuit.




# Ammeter Insertion Effect

- Placing the meter in series with  $R_1$  causes the current to reduce to a value equal to:

$$I_m = \frac{E}{R_1 + R_m} \quad (2)$$

- Dividing equation (2) by (1) yields:

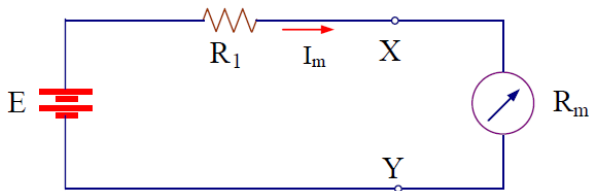
$$\frac{I_m}{I_e} = \frac{R_1}{R_1 + R_m} \quad (3)$$


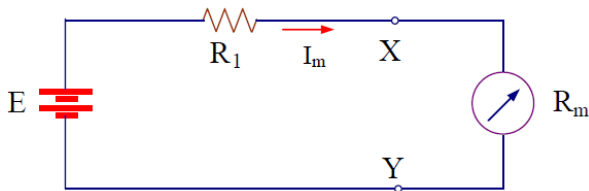
# Ammeter Insertion Effect


- The Ammeter insertion error is given by:

$$\text{Insertion Error} = \left(1 - \frac{I_m}{I_e}\right) \times 100\% \quad (4)$$



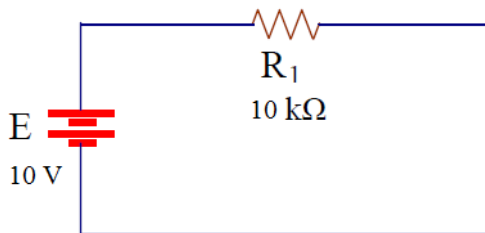
## Example 4

A current meter that has an internal resistance of  $2\text{ k}\Omega$  is used to measure the current through  $R_1$  in the following Figure. Determine the percentage of error of the reading due to ammeter insertion.


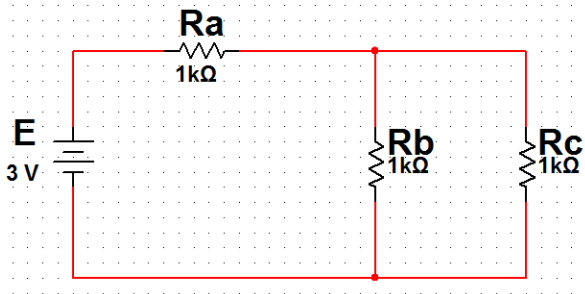
## Example 5


A current meter that has an internal resistance of  $78\ \Omega$  is used to measure the current through  $R_c$  in the following Figure. Determine the percentage of error of the reading due to ammeter insertion.




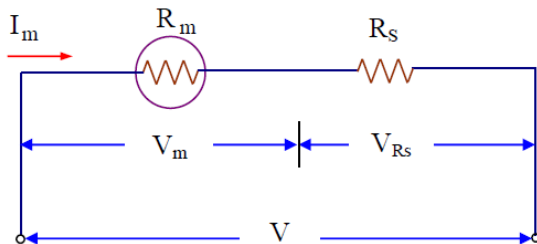
## 5. D'Arsonval Meter as DC Voltmeter


- The basic D'Arsonval meter movement can be converted to a **DC Voltmeter** by connecting a multiplier  $R_s$  in series with the meter movement as shown in Figure.
- The purpose of the multiplier:
  - 1 is to extend the voltage range of the meter.
  - 2 to limit current through the d'Arsonval meter movement to a maximum full-scale deflection current.


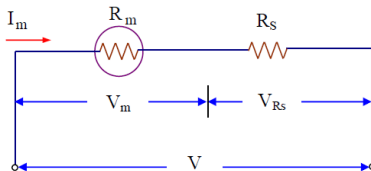
# D'Arsonval Meter as DC Voltmeter

- To find the value of the multiplier resistor, first determine the **sensitivity,  $S$** , of the meter movement.

$$S = \frac{1}{I_{fs}} (\Omega/V) \quad (5)$$



- where;  
 $I_m$ : full scale deflection current of the movement ( $I_{fs}$ ).  
 $R_m$ : internal resistance of the movement.  
 $R_s$ : multiplier resistance.  
 $V$ : full range voltage of the instrument.

# D'Arsonval Meter as DC Voltmeter


- From the circuit of Figure below

$$V = I_m(R_s + R_m) \quad (6)$$

$$R_s = \frac{V - I_m R_m}{I_m} = \frac{V}{I_m} - R_m \quad (7)$$

$$R_s = S.V - R_m \quad (8)$$
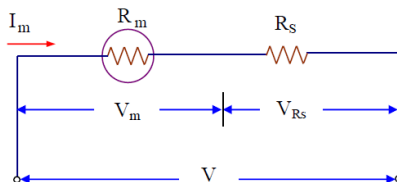
$$R_s = \text{Sensitivity} \cdot \text{Range} - \text{Internal Resistance} \quad (9)$$




## Example 6

Calculate the value of the multiplier resistance on the 50 V range of a DC voltmeter that used a  $500\ \mu\text{A}$  meter movement with an internal resistance of  $1\text{k}\Omega$ .

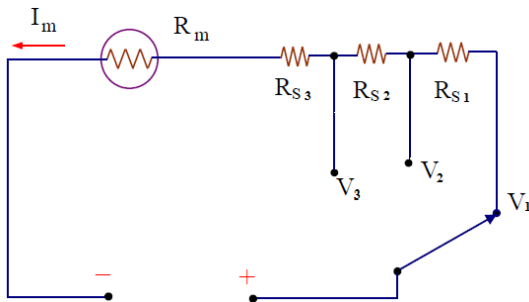
## 6. Multi-Range DC Voltmeter

- A DC voltmeter can be converted into a multi-range DC voltmeter by connecting a number of resistors (multipliers) in series with the meter movement.
- A practical multi-range DC voltmeter is shown in Figure.


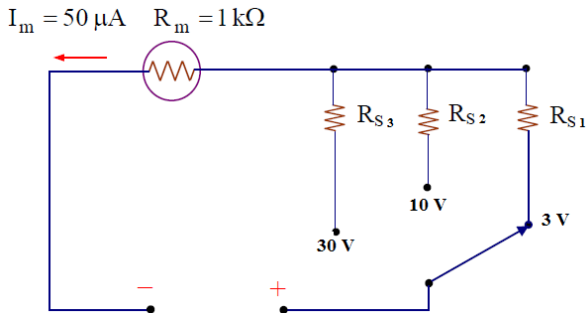
## Example 7


Calculate the value of the multiplier resistance for the multiple-range DC voltmeter circuit shown in the Figure.


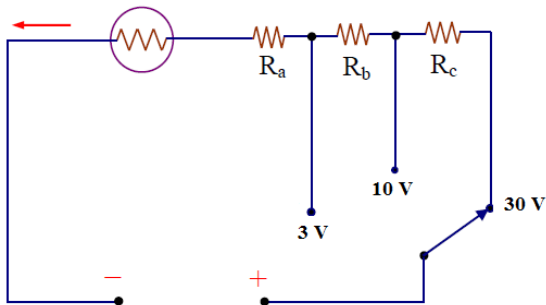
## Example 8

Calculate the value of the multiplier resistance for the multiple-range DC voltmeter circuit shown in the Figure.

$$I_m = 50 \mu\text{A} \quad R_m = 1 \text{ k}\Omega$$



## 7. Voltmeter Loading Effects

- When a voltmeter is used to measure the voltage across a circuit component, the voltmeter circuit itself is in parallel with the circuit component.
- Total resistance will decrease, so the voltage across component will also decrease. This is called voltmeter loading.
- The resulting error is called a **loading error**.
- The voltmeter loading can be reduced by using a high sensitivity voltmeter.

$$\text{Voltmeter Error} = \frac{\text{Expected value} - \text{Measured value}}{\text{Expected value}} \times 100\% \quad (10)$$



## Example 9

Two different voltmeters are used to measure the voltage across resistor  $R_B$  in the circuit of the Figure. The meters are as follows.

Meter A:  $S = 1\text{k}\Omega/\text{V}$ ,  $R_m = 0.2\text{k}\Omega$ , range = 10V

Meter B:  $S = 20\text{k}\Omega/\text{V}$ ,  $R_m = 1.5\text{k}\Omega$ , range = 10V

Calculate:

- 1 Voltage across  $R_B$  without any meter connected across it.
- 2 Voltage across  $R_B$  when meter A is used.
- 3 Voltage across  $R_B$  when meter B is used.
- 4 Error in voltmeter readings.




## 8. The Ohmmeter

- The ohmmeter consists of battery, resistor and meter movement.
- The full-scale deflection current is,

$$I_{fs} = \frac{E}{R_z + R_m} \quad (11)$$

where,  $R_z$ : variable resistor

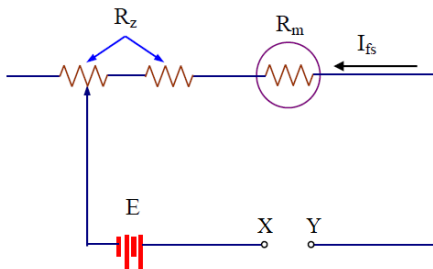- To determine the value of unknown resistor,  $R_x$ . The  $R_x$  is connected to terminal X and Y.



# The Ohmmeter

- The circuit current is now expressed,

$$I = \frac{E}{R_z + R_m + R_x} \quad (12)$$

- The current  $I$  is less than the full-scale current  $I_{fs}$ , because of the addition resistance  $R_x$
- If  $R_x = R_z + R_m$

$$I = \frac{E}{2(R_z + R_m)} = \frac{1}{2} I_{fs} \quad (13)$$

- If  $R_x = 2(R_z + R_m)$

$$I = \frac{E}{3(R_z + R_m)} = \frac{1}{3} I_{fs} \quad (14)$$

# The Ohmmeter

- If  $R_x = 3(R_z + R_m)$

$$I = \frac{E}{4(R_z + R_m)} = \frac{1}{4} I_{fs} \quad (15)$$

- The ratio of the current,  $I$  to the full-scale deflection current,  $I_{fs}$  is

$$\frac{I}{I_{fs}} = \frac{R_z + R_m}{R_z + R_m + R_x} \quad (16)$$

- If we let  $P$  represent the ratio of the current  $I$  to the full-scale deflection current,  $I_{fs}$ . We can say that

$$P = \frac{I}{I_{fs}} = \frac{R_z + R_m}{R_z + R_m + R_x} \quad (17)$$

## Example 10

An ohmmeter uses a 1.5 V battery and a basic 50  $\mu\text{A}$  movement and  $R_m$  of 100  $\Omega$ . Calculate

- 1 the value of  $R_z$  required
- 2 the value of  $R_x$  that would cause half-scale deflection in the circuit.

## Example 11

A 1 mA full-scale deflection current meter movement is to be used in an ohmmeter circuit. The meter movement has an internal resistance,  $R_m$  of  $100\ \Omega$  and a 3 V battery will be used in the circuit. Mark off the meter face for reading resistance.